



## HANDHELD CALCULATOR BATTERY SYSTEMS

### INTRODUCTION

Batteries suitable for handheld calculator applications can be categorized into two groups: primary cells and secondary cells. Primary cells cannot be recharged efficiently or safely and are used in "throw away" systems, i.e., the end user must replace the calculator batteries at end of life. Secondary cells can be recharged after being discharged under specified conditions.

### PRIMARY CELLS

Carbon-zinc and alkaline are the best known non-rechargeable cells available for calculators. Carbon-zinc cells are low cost, but have relatively high internal resistance characteristics that reduce efficiency under high current drain conditions. They are widely available around the world in a variety of voltages, capacity, and form factor options. Alkaline cells offer 300 to 400 per cent more capacity than carbon-zinc batteries of the same size and have excellent characteristics under the high drain conditions typical of LED display calculators. Both types have voltage discharge curves that fall gradually over life. Shelf life for alkaline is good, carbon-zinc poor; an important parameter if batteries are to be shipped with the finished calculator and may sit on warehouse or display shelves for unknown periods of time. Not surprisingly, alkaline cells are also three to four times more expensive than carbon-zinc. Silver oxide batteries have been used in throw-away calculator applications to achieve a more desirable form factor. Although replacements are available (the cells are often used in hearing aids and cameras) the high current drain inefficiency of the cell results in poor utilization of available capacity, and battery life is short.

### SECONDARY CELLS

Nickel-cadmium batteries have become the standard for rechargeable systems. They exhibit relatively constant discharge voltages and can be recharged many times. Internal resistance is low so they are capable of supplying high peak currents.

Figure 1 indicates the discharge characteristics of carbon-zinc, alkaline and nickel-cadmium cells.

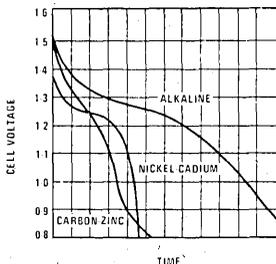


Figure 1. Comparison of Discharge Characteristics

### THE SIMPLEST SYSTEM — A 9 V BATTERY

Most National Semiconductor calculator circuits use a P-channel, metal gate MOS process with enhancement and depletion mode transistors. They are designed to operate directly from a nine volt alkaline or carbon-zinc battery. Operating voltage range is 6.5 V to 9.5 V. A nine volt battery is simply six series cells with characteristics similar to those shown in Figure 1, allowing an end-point voltage for each cell of just under 1.1 V for a worst-case calculator.

A complete calculator using a nine volt battery is shown in Figure 2. This is undoubtedly the simplest battery system available for a low cost calculator, as well as being the most efficient. The current required to drive the display and MOS circuit comes directly from the battery without any conversion of voltage.

Battery life estimates are straightforward. Assuming a nine digit calculator using the National MM5760 slide rule chip, and five "8s" as a typical display condition, it is easy to calculate total battery current drain and battery life:

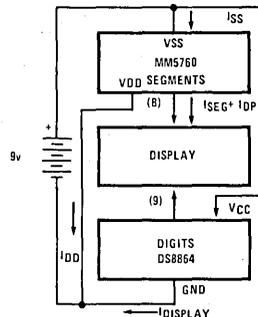


Figure 2. Power Supply Current for 9 V Calculator

Referring to Figure 2 and using typical values from the 5760 data sheet,

$$I_{\text{DISPLAY}} = I_{\text{SEG}}(\text{Ave}) + I_{\text{DP}}(\text{Ave})$$

$$= (I_{\text{SEG}}) \left( \frac{\text{no. of segments}}{\text{on per digit}} \right) \left( \frac{\text{no. of digits}}{\text{on per word}} \right) \left( \frac{\text{Digit Duty}}{\text{Cycle}} \right) + I_{\text{DP}}$$

where  $I_{\text{SEG}}$  = Peak Segment Current

$$\text{Digit Duty Cycle} = \frac{(\text{Digit Time}) - (\text{Segment Blanking Time})}{(\text{Word Time})}$$

$$= \frac{70 \mu\text{s} - 4.5 \mu\text{s}}{650 \mu\text{s}} \sim 0.100$$

Therefore, for a display of five "8s:"


$$I_{\text{DISPLAY}} = \left( \frac{8.5 \text{ mA}}{\text{Seg}} \right) \left( \frac{7 \text{ Seg}}{\text{Digit}} \right) (5 \text{ digits}) (0.100)$$

$$= 29.75 \text{ mA}$$


$$I_{\text{BATTERY DRAIN}} = I_{\text{SS}} = I_{\text{DD}} + I_{\text{DISPLAY}}$$
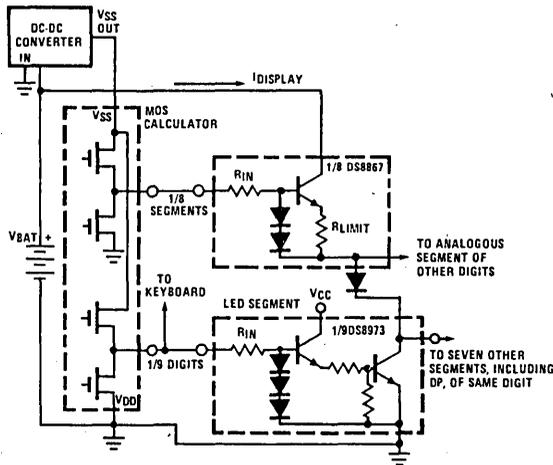
$$= 8.0 \text{ mA} + 29.8 \text{ mA} = 37.8 \text{ mA}$$





(a)

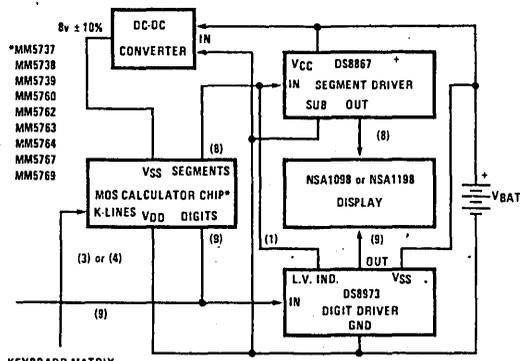

(b)

Figure 4 (a) Schematic Diagram, and (b) Block Diagram

With the exception of the MM5758 which is designed specifically to operate with a three cell battery system, all other National Semiconductor single chip calculators have low impedance segment output buffers suitable for driving LEDs directly. In a three cell system they will be capable of over-driving the DS8867. Typical input current to the DS8867 is about 1.5 mA per segment, which unfortunately must be converted up to the V<sub>SS</sub> supply and therefore does impact battery life to some degree.

Typical battery drain for a display of five "8s" in a three cell system is:

$$I_{BAT} \cong \left[ I_{DDMOS} + (I_{SEG DRIVE MOS}) \left( \frac{\text{Digit Duty}}{\text{Cycle}} \right) \left( \frac{\text{no. of}}{\text{segments on}} \right) \right] \cdot \frac{V_{CONVERTER}}{V_{BAT} \cdot \text{EFF}_{CONVERTER}} + I_{SEG BAT} \left( \frac{\text{Digit Duty}}{\text{Cycle}} \right) \cdot \left( \frac{\text{no. of}}{\text{segments on}} \right)$$

$$I_{BAT} \cong \left[ 8 \text{ mA} + (1.5 \text{ mA}) \left( \frac{5}{9} \right) (7) \right] \frac{8.0}{(3.6) (0.75)} + (17 \text{ mA}) (0.1) (5 \text{ digits}) \left( \frac{7 \text{ seg}}{\text{Digit}} \right)$$

$$= 100.49 \text{ mA}$$

Using three AA alkaline cells would give a battery life of (1500 mA-hr/100.5 mA), or almost 15 hours; a 56% improvement over the two cell system for the additional cost of the DS8867 and an additional battery. 500 mA/hr ni-cad cells would provide 5.0 hours of continuous life. Note that this extended battery life is with higher display current than the two cell system, which will result in a brighter display as an added bonus.

#### FOUR CELL SYSTEM

A four cell battery system offers even higher power efficiency than the three cell system and the additional battery cost is offset somewhat by the removal of the DS8867. If the DC-DC converter output voltage is regulated between V<sub>SS</sub> - 7.5 V and V<sub>SS</sub> - 9.5 V, segments can be driven directly (Figure 5). Figure 6 shows the system diagram.

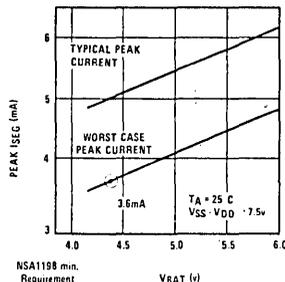


Figure 5. Guaranteed Peak Display Current vs. Battery Voltage in a Four Cell Battery System.

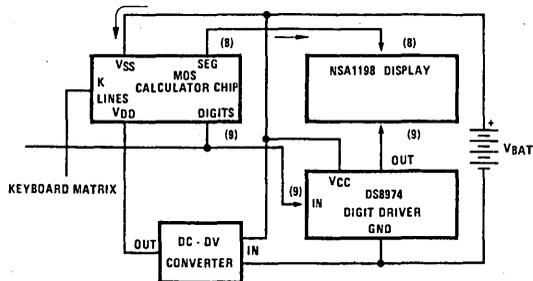


Figure 6. Four Cell Battery System

Like the three cell system, only the calculator supply needs to be converted up from the battery voltage. The display current flows in a loop from the positive terminal of the batteries, through V<sub>SS</sub> and the segment buffers of the calculator chip to the LED, then the digit driver and back to the negative side of the batteries.

Battery drain current with five "8s" displayed is:

$$I_{BAT} = I_{DDMOS} \left( \frac{V_{CONVERTER}}{V_{BAT} \cdot \text{EFF}_{CONVERTER}} \right) + I_{DISPLAY}$$

$$\cong (10 \text{ mA}) \left[ \frac{8.75}{(4.8)(0.75)} \right] + \left( \frac{8.5 \text{ mA}}{\text{seg}} \right) \left( \frac{7 \text{ seg}}{\text{Digit}} \right) (5 \text{ Digits}) (0.1)$$

$$= 54.0 \text{ mA}$$

Using four AA cells would give a battery life of at least (1500 mA-hr/54.0 mA), or almost 28 hours of continuous use. Four smaller capacity cells could be used to improve the form factor of the finished calculator and still maintain a reasonable battery life. For example, four alkaline N cells would give almost 10 hours of operation.

Table 1.

No. of Battery Cells	Calculator Type	Segment Driver	Digit Driver	DC-DC Converter	Typical Battery Life with AA Alkaline Cells
2	Group A	None	DS8872	$2.0 \text{ V} \leq V_{IN} \leq 3.0 \text{ V}$ $6.5 \text{ V} \leq V_{OUT} \leq 9.5 \text{ V}$ $I_{OUT} \leq -125 \text{ mA}$	9.6 hours
2	Group B	None	DS8874	$2.0 \text{ V} \leq V_{IN} \leq 3.0 \text{ V}$ $6.5 \text{ V} \leq V_{OUT} \leq 9.5 \text{ V}$ $I_{OUT} \leq -125 \text{ mA}$	7.7 hours
3	Group A	DS8867	DS8872 or DS8973	$3.0 \text{ V} \leq V_{IN} \leq 4.5 \text{ V}$ $7.2 \text{ V} \leq V_{OUT} \leq 8.8 \text{ V}$ $I_{OUT} \leq 20 \text{ mA}$	15.0 hours
3	Group B	DS8867	DS8879	$3.0 \text{ V} \leq V_{IN} \leq 4.5 \text{ V}$ $7.2 \text{ V} \leq V_{OUT} \leq 8.8 \text{ V}$ $I_{OUT} \leq -20 \text{ mA}$	15.0 hours
3	MM5758	DS8867	DS8868	$3.0 \text{ V} \leq V_{IN} \leq 4.5 \text{ V}$ $7.2 \text{ V} \leq V_{OUT} \leq 8.8 \text{ V}$ $I_{OUT} \leq -25 \text{ mA}$	14.5 hours
4	Group A	None	DS8872 or DS8974	$4.4 \text{ V} \leq V_{IN} \leq 6.0 \text{ V}$ $-7.5 \text{ V} \leq V_{OUT} \leq -9.5 \text{ V}$ $I_{OUT} \leq 20 \text{ mA}$	28.0 hours
4	Group B	None	DS8876	$4.4 \text{ V} \leq V_{IN} \leq 6.0 \text{ V}$ $-7.5 \text{ V} \leq V_{OUT} \leq -9.5 \text{ V}$ $I_{OUT} \leq 20 \text{ mA}$	23.5 hours
9 V	Group A	None	DS8873 or DS8864	None	14.0 hours
9 V	Group B	None	DS8874	None	11.3 hours

## Group A Calculators

MM5737 MM5762  
MM5738 MM5763  
MM5739 MM5764  
MM5760 MM5767  
MM5769

## Group B Calculators

MM5784  
MM5791